




成功大學

National Cheng Kung University

Verilog Basics - Behavioral Model

 
Original by Thanasis Oikonomou
Modified by Ing-Chao Lin





Outline


 
- Procedures
 - Initial
 - Always
- Procedural Statements
 - if-else
 - case
 - for
- Mixed Model



Behavioral Model - Procedures (i)



  
- **always** and **initial**
- Procedures = sections of code that we know they execute sequentially
- Procedural statements = statements inside a procedure (they execute sequentially)
- e.g. another 2-to-1 mux implem:



Behavioral Model - Procedures (ii)



 - Modules can contain any number of procedures
- Procedures execute in parallel (in respect to each other) and ..
- .. can be expressed in two types of blocks:
 - initial → they execute only once
 - always → they execute for ever (until simulation finishes)



“Initial” Blocks

- Start execution at sim time zero and finish when their last statement executes

```
module first;
```

```
initial
```

```
    $display("I'm first"); ←
```

Will be displayed
at sim time 0

```
initial begin
```


```
    #50;
```

```
    $display("Really?"); ←
```

Will be displayed
at sim time 50

```
end
```



```
endmodule
```

 



“Always” Blocks

 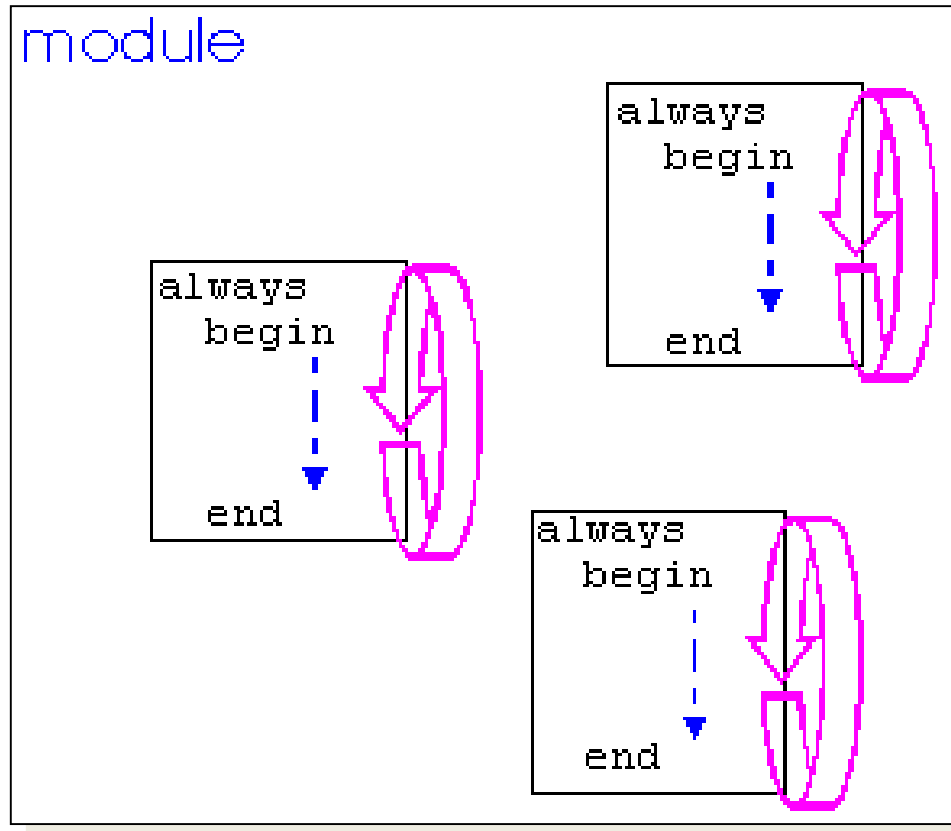- Start execution at sim time zero and continue until sim finishes





Events

- @

```
always @(signal1 or signal2 or ..) begin  
    ..  
end
```


execution triggers every
time any signal changes

```
always @(posedge clk) begin  
    ..  
end
```

execution triggers every
time clk changes
from 0 to 1

```
always @(negedge clk) begin  
    ..  
end
```

 execution triggers every
time clk changes
from 1 to 0



Examples




- Half adder implem

```
module half_adder(S, C, A, B);  
output S, C;  
input A, B;  
  
reg S,C;  
wire A, B;  
  
always @(A or B) begin  
    S = A ^ B;  
    C = A && B;  
end  
  
endmodule
```


- Behavioral edge-triggered DFF implem
 
```
module dff(Q, D, Clk);  
output Q;  
input D, Clk;  
  
reg Q;  
wire D, Clk;  
  
always @(posedge Clk)  
    Q = D;  
  
endmodule
```






Example

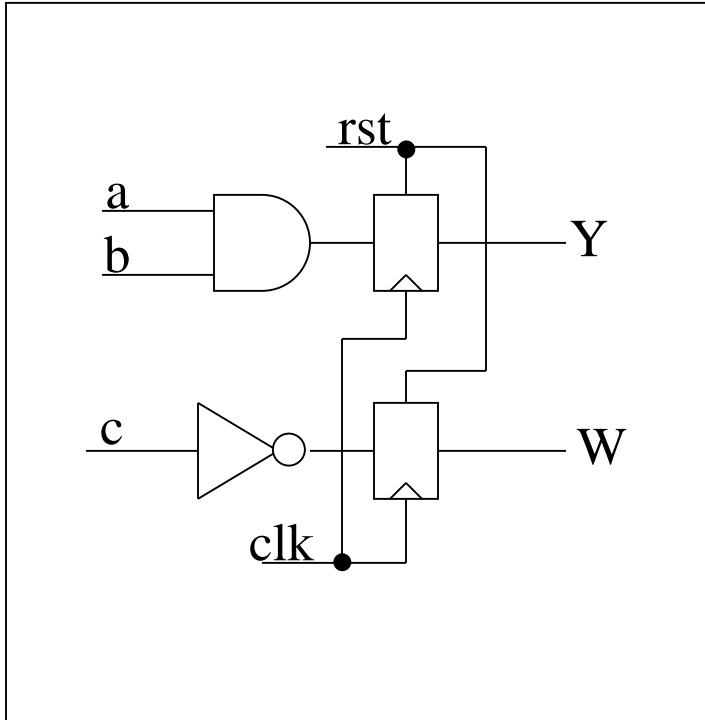
 
```
always @(posedge rst or posedge clk)
begin
    if (rst) begin
        Y = 0;
        W = 0;
    end
    else begin
        Y = a & b;
        W = ~c;
    end
end
end
```






Procedural Assignments

- Blocking Assignment (use =)
- Nonblocking Assignment (use <=)

```
// Blocking assignments
initial begin
a = #10 1'b1; // The simulator assigns 1 to a at time 10
b = #20 1'b0; // The simulator assigns 0 to b at time 30
c = #40 1'b1; // The simulator assigns 1 to c at time 70
end

 // Nonblocking assignments
initial begin
d <= #10 1'b1; // The simulator assigns 1 to d at time 10
e <= #20 1'b0; // The simulator assigns 0 to e at time 20
f <= #40 1'b1; // The simulator assigns 1 to f at time 40
end
```



Procedural Statements: if



```
if (expr1) begin
    true_stmt1;
end

else if (expr2) begin
    true_stmt2;
    ..
end

else begin
    def_stmt;
end
```


E.g. 4-to-1 mux:

```
module mux4_1(out, in, sel);
    output out;
    input [3:0] in;
    input [1:0] sel;

    reg out;
    wire [3:0] in;
    wire [1:0] sel;

    always @(in or sel)
        if (sel == 0)
            out = in[0];
        else if (sel == 1)
            out = in[1];
        else if (sel == 2)
            out = in[2];
        else
            out = in[3];

endmodule
```

 



Procedural Statements: case

```
case (expr)

item_1: stmt1;
item_2: stmt2;
..
default:
    def_stmt;


endcase
```

E.g. 4-to-1 mux:

```
module mux4_1(out, in, sel);
output out;
input [3:0] in;
input [1:0] sel;

reg out;
wire [3:0] in;
wire [1:0] sel;

 always @(in or sel)
    case (sel)
    0: out = in[0];
    1: out = in[1];
    2: out = in[2];
    3: out = in[3];
    default: out = in[0];
    endcase
endmodule
```





Procedural Statements: for

```
for (init_assignment; cond; step_assignment)
    stmt;
```

E.g.


```
module count(sum, Y, clk);
output [3:0] sum;
input clk, Y;

reg [3:0] Y [0:2];
integer i;

assign sum = Y[0] + Y[1] + Y[2];

always @(posedge clk)
    for (i = 0; i < 3; i = i + 1)
        Y[i] = Y[i] + 1;

endmodule
```

 



Mixed Model



Code that contains various both structure and behavioral styles

```
Module simple(Y, c, clk, rst);  
Output Y;  
Input c, clk, rst;
```

```
Reg Y;  
Wire c, clk, rst;  
Wire n;
```

```
Not(n, c); // gate-level
```
 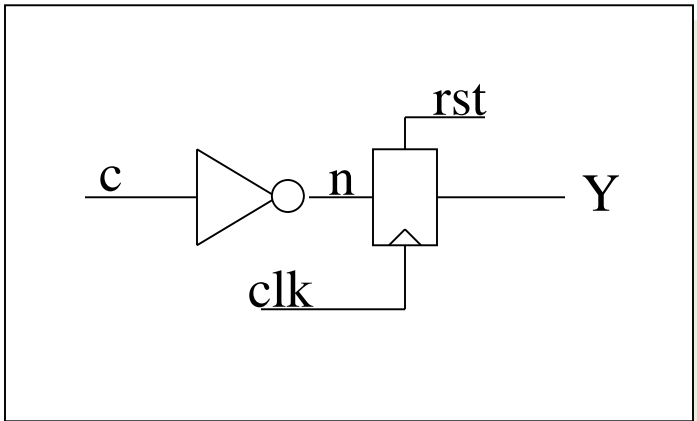
```
Always @(res or posedge clk)  
    if (rst)  
        Y = 0;  
    else  
        Y = n;  
endmodule
```





成功大學

National Cheng Kung University

Backup slides

