



成功大學

National Cheng Kung University


Combinational Logic Modules

Source:

Digital System Designs and Practices Using Verilog HDL and FPGAs


@ 2008, John Wiley

 Partial from Digital IC Design, By Pei-Yin Chen






Outline

 - Combinational Circuit vs. Sequential Circuit
- Parameter
- Basic Combinational Logic Modules
- Options for Modeling Combinational Logic




Combinational Circuit

   - A combinational circuit: Outputs at any time are determined directly from the present combination of inputs without regard to previous inputs.




Sequential Circuit

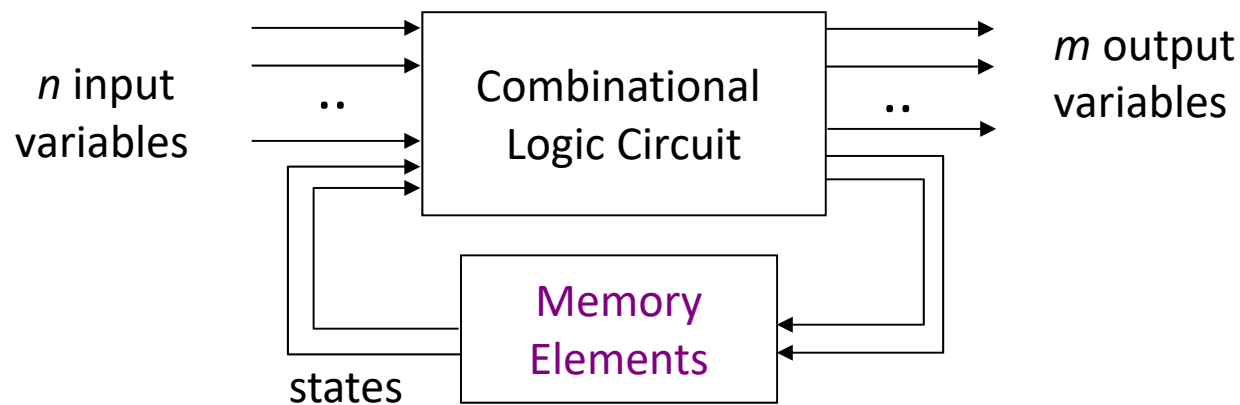A sequential circuit is a system whose outputs at any time are determined from the present combination of inputs and the previous states.



- Sequential components contain memory elements

 Ex: Ring counter that starts the answering machine after 4 rings



Parameter

- Parameter declaration

parameter identifier = constant_expression ,


- You can use a parameter anywhere that you can use a literal.

```
module mod(ina, inb, out);  
.....  
  
parameter m1=8;  
.....  
  
wire [m1:0] w1;  
.....  
  
endmodule
```

w1 can be set as a (n+1)-bit wire if we change m1 to n

(i.e., m1=10 → w1 becomes a 11-bit wire

m1=4 → w1 becomes a 5-bit wire)

 


Parameterized Design (1/2)

```
module test (a, b, c);  
parameter width = 8;  
input [width - 1 : 0] a, b;  
output [width - 1 : 0] c;  
  
assign c = a & b;  
  
endmodule
```

```
module PARAM(A, B, C);  
input [3:0] A, B;  
output [3:0] C;  
wire f;  
  
or o1(f, A, B);  
test#(4) u1(A, f, C);  
  
endmodule
```

Override the value of width when the test module is instantiated
Save the file as PARAM.v and compile (synthesis) it

➔ the width value become 4

 


Parameterized Design (2/2)



```
module test_2(A, B, C, D);  
parameter width = 8;  
parameter height = 8;  
parameter length = 8;  
  
input [width - 1 : 0] A;  
input [height - 1 : 0] B;  
input [length - 1 : 0] C;  
output [width : 0] D;  
  
assign D = A + B + C;  
  
endmodule
```

```
module PARAM_1(A, B, C, D);  
input [4 : 0] A;  
input [3 : 0] B;  
input [3 : 0] C;  
output [5 : 0] D;  
  
test_2#(5, 4, 4) u1(A, B, C, D);  
  
endmodule
```

 
Override those values of many parameters when the test_2 module is instantiated (**width = 5; height = 4; length = 4**)



Basic Combinational Logic Modules





 - Commonly used combinational logic modules:
 - Multiplexer
 - Decoder
 - Encoder
 - Comparator
 - Adder
 - Subtractor
 - Multiplier
 - Arithmetic Logic Unit(ALU)



An n -bit 4-to-1 Multiplexer Example

```
// an N-bit 4-to-1 multiplexer using conditional operator.  
module mux_nbit_4to1(select, in3, in2, in1, in0, y);  
parameter N = 4; // define the width of 4-to-1 multiplexer  
input [1:0] select;  
input [N-1:0] in3, in2, in1, in0;  
output [N-1:0] y;  
// the body of the N-bit 4-to-1 multiplexer  
assign y = select[1] ?  
    (select[0] ? in3 : in2) :  
    (select[0] ? in1 : in0);  
endmodule
```

 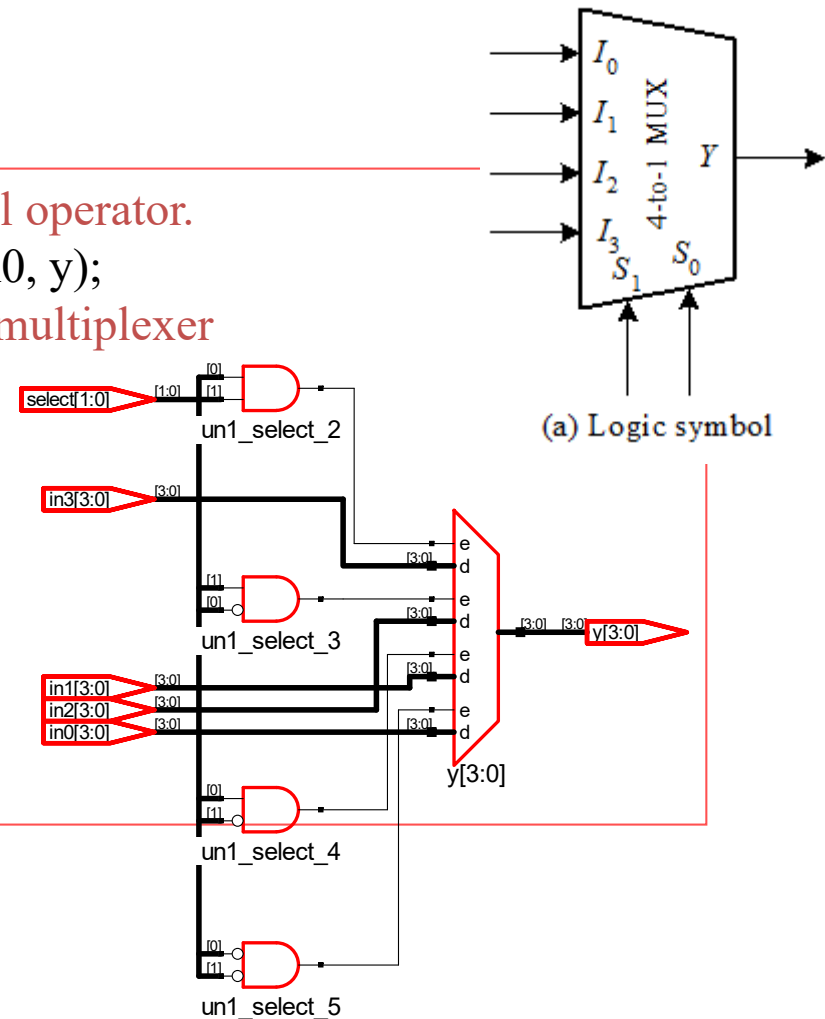

A 2-to-4 Decoder Example

// a 2-to-4 decoder with active low output

```
module decoder_2to4_low(x,enable,y);
```

```
input [1:0] x;
```

```
input enable;
```

```
output reg [3:0] y;
```

// the body of the 2-to-4 decoder

```
always @(x or enable)
```

```
if (enable) y = 4'b1111; else
```

```
case (x)
```

```
2'b00 : y = 4'b1110;
```

```
2'b01 : y = 4'b1101;
```



```
2'b10 : y = 4'b1011;
```

```
2'b11 : y = 4'b0111;
```

```
default : y = 4'b1111;
```

```
endcase
```

```
endmodule
```

  

Options for Modeling Combinational Logic



- Options for modeling combinational logic:
 - Verilog HDL primitives
 - Ex: `and (a, b, c)`
 - Continuous assignment
 - Ex: `assign out = i1& i2;`
 - Behavioral statement
 - `always` statement

